

# **Lab 1 Report**

ECE 124

Group 17 Session 204


**Justin Aujla**

**Yuhao Chen**


## Screenshot of VHDL Polarity Control

```
1  -- Author: Group 17, Justin Aujla, Yuhao Chen
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  LIBRARY work;
5
6  ENTITY VHDL_polarity_ctrl IS
7  PORT(
8      POLARITY_CNTRL, IN_1, IN_2, IN_3, IN_4 : IN STD_LOGIC;
9      OUT_1, OUT_2, OUT_3, OUT_4 : OUT STD_LOGIC
10 );
11 END VHDL_polarity_ctrl;
12
13 ARCHITECTURE dataflow OF VHDL_polarity_ctrl IS
14 BEGIN
15     OUT_1 <= POLARITY_CNTRL XOR IN_1;
16     OUT_2 <= POLARITY_CNTRL XOR IN_2;
17     OUT_3 <= POLARITY_CNTRL XOR IN_3;
18     OUT_4 <= POLARITY_CNTRL XOR IN_4;
19 END dataflow;
```
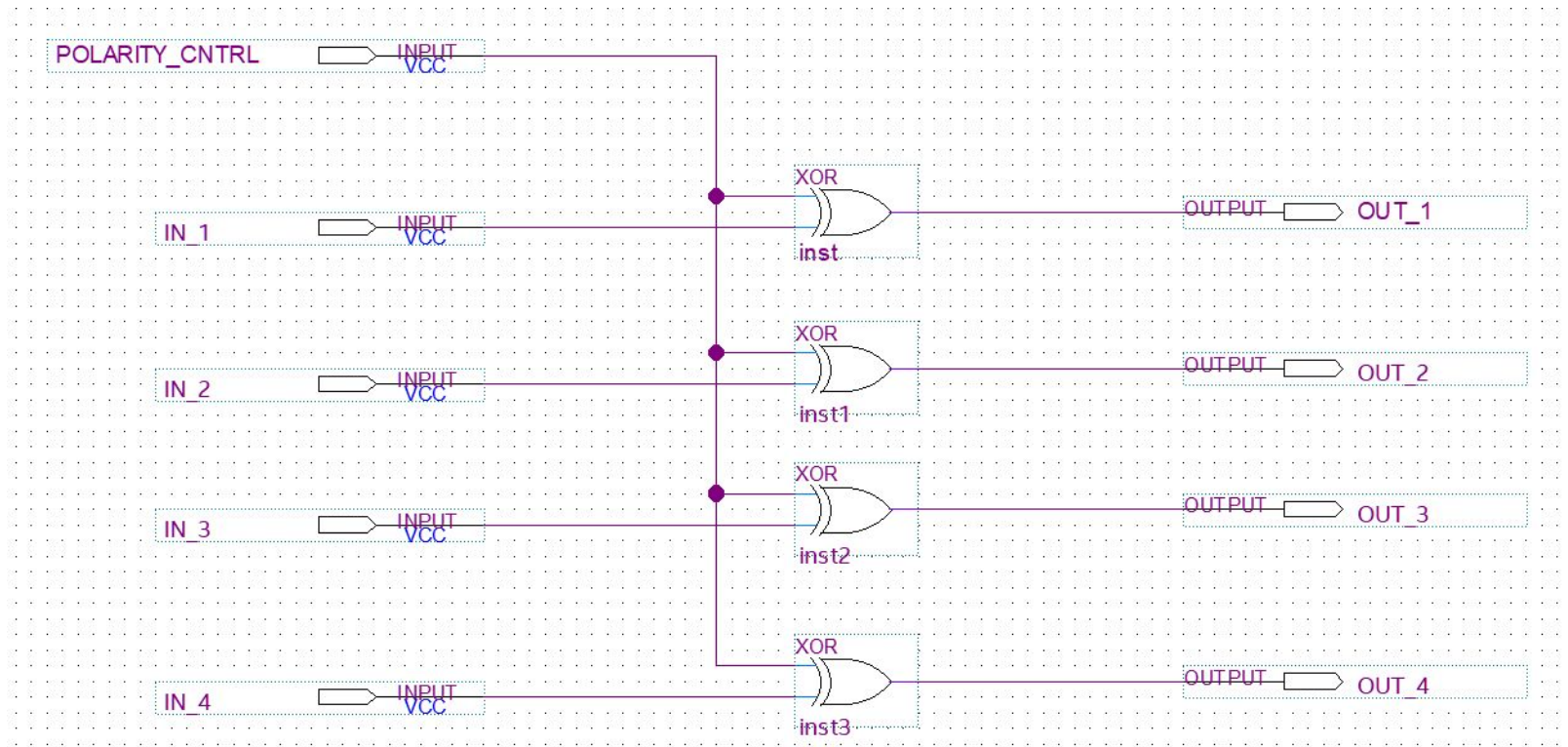
## Screenshot of Schematic Polarity Control



 Simulation with Annotation (sw[1] set to low)



## Simulation with Annotation (sw[1] set to high)

